


Speaker impedance in parallel

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{R_T}$$

$$\frac{1}{4 \text{ ohms}} + \frac{1}{8 \text{ ohms}} + \frac{1}{16 \text{ ohms}} = \frac{1}{R_T}$$

$$\frac{4}{16} + \frac{2}{16} + \frac{1}{16} = \frac{7}{16} = 0.4375$$

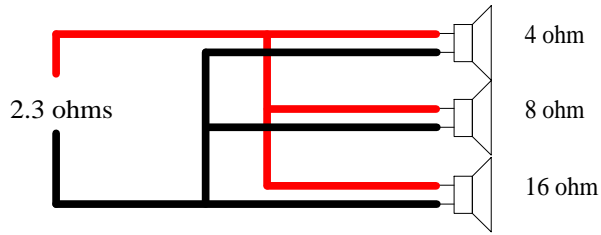
$$\frac{1}{0.4375} = 2.2857 \quad R_T = 2.3 \text{ ohms}$$



Speaker impedance in series

$$R_1 + R_2 = R_T$$
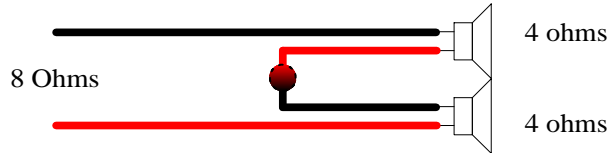
$$4 \text{ ohms} + 4 \text{ ohms} = 8 \text{ ohms}$$



Speaker impedance in series parallel

$$R_1 + R_2 = R_T$$

$$4 \text{ ohms} + 4 \text{ ohms} = 8 \text{ ohms}$$

$$R_1 + R_2 = R_T$$

$$4 \text{ ohms} + 4 \text{ ohms} = 8 \text{ ohms}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_T}$$

$$\frac{1}{8 \text{ ohms}} + \frac{1}{8 \text{ ohms}} = \frac{1}{R_T}$$

$$\frac{1}{8} + \frac{1}{8} = \frac{2}{8} = \frac{1}{4} = 0.25$$

$$\frac{1}{0.25} = 4 \text{ ohms}$$

